

Digital Logic

2069

Full Marks : 60

Pass Marks : 24

Time : 3 hrs.

Long answer questions :

Attempt any two questions :

(2*10=20)

- 1.) What is decoder? Implement the following using decoder.
 - a.) $F(W X Y Z) = \sum (0,1,3,4,8,9,10)$
 - b.) $F(W X Y Z) = \sum (1,3,5,6,11,13,14)$
- 2.) What do you mean by asynchronous counter? Design a mod-6 synchronous counter using T flip-flops.
- 3.) Explain the Master-slave S-R flip-flop with logic diagram, truth table and timing diagram.

Short answer questions :

Attempt any eight questions :

(8*5=40)

- 4.) Design a half subtractor using only NOR gates.
- 5.) Convert the following decimal numbers into hexadecimal and octal number.
 - a.) 220
 - b.) 1020
- 6.) Design a multiplexer 4*1 using only universal gates.
- 7.) What is J-K flip flop? Explain.
- 8.) Write a procedure to reduce K-maps.
- 9.) What are the various types of shift registers?
- 10.) Draw a logic diagram of a 4 bit ripple counter using D-flip flop.
- 11.) Differentiate between combinational logic and sequential logic. List some applications of sequential logic.
- 12.) Explain the decimal adder.
- 13.) Write short notes on :
 - a.) Programmable Logic Array
 - b.) Triggering at flip-flop
 - c.) Memory Unit